

# Lab 3: Report

---


**Name:** Paul Blair, Benjamin Drumwright

**NetID:** VBQ669, DRUM


We built the circuits together and both worked on the code. Ben wrote the code for part 2 and Paul wrote the code for part 1. We worked on part 3 together.

## R1

---

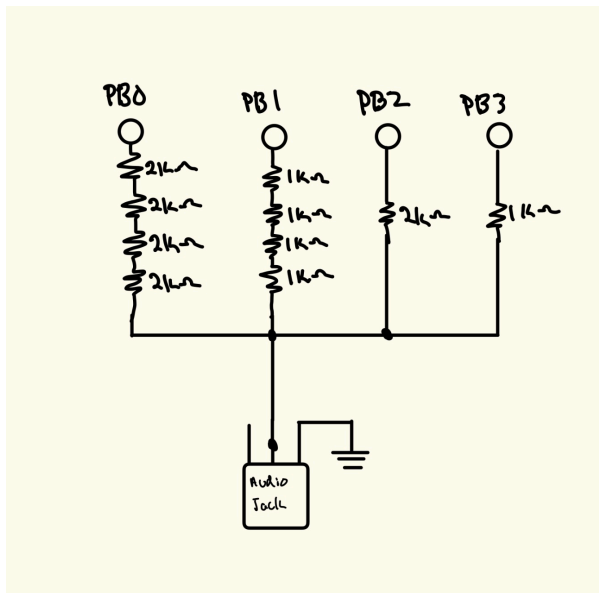

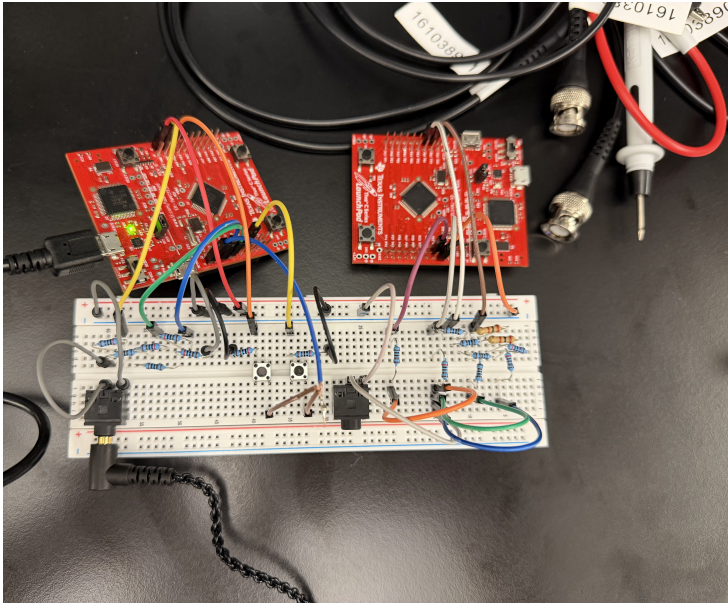Circuit for R1 (On the left) and R2 (On the Right)



Note about the circuits: we didn't have the correct resistors so we used 1k and 2k resistors in series to get to the correct resistance values.

## R2

